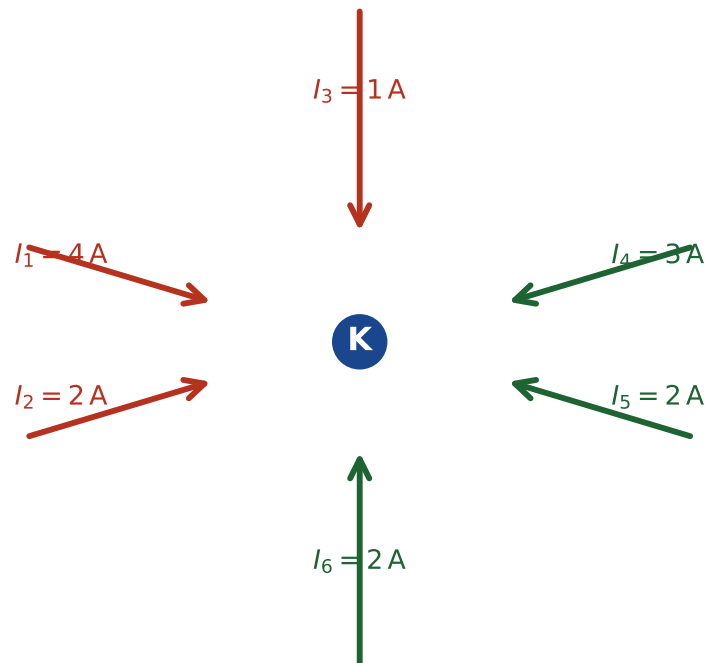


Elektrischer Knoten

$$\sum I_{\text{zu}} = \sum I_{\text{ab}}$$



■ Zustrom $\Sigma = 7 \text{ A}$
■ Abstrom $\Sigma = 7 \text{ A}$

Stromstärken am Knoten

$$\sum_k I_k = 0$$

