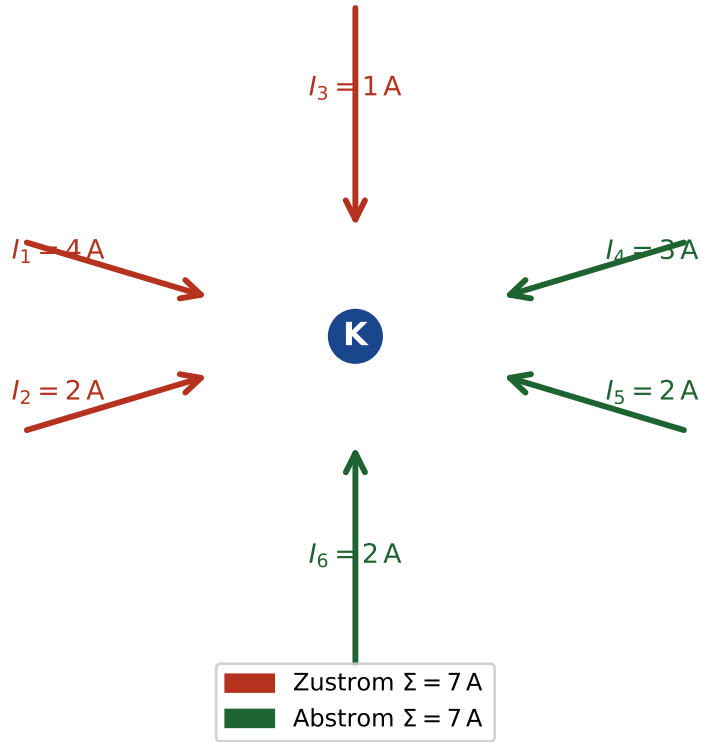


Elektrischer Knoten

$$\sum I_{\text{zu}} = \sum I_{\text{ab}}$$



Stromstärken am Knoten

$$\sum_k I_k = 0$$

